








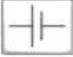
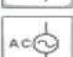

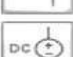
GANDHI SCHOOL OF  
ENGINEERING, BHABANDHA, BERHAMPUR

# **TEACHING AND LEARNING MATERIAL**





**SUBJECT: CIRCUIT NETWORK THEORY**  
**SEMESTER: 3<sup>RD</sup>**

## CHAPTER-1


### DIFFERENT TYPES OF POWER SOURCE

Power sources	
	Battery
	Battery with polarity labels
	Ideal current source
	Ideal voltage source
	Oscillator
	AC current source
	AC voltage source
	DC current source
	DC voltage source


## DIFFERENT TYPES OF SOURCE

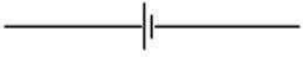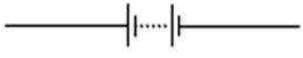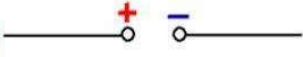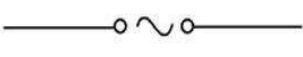Cell	
Battery	
Direct Current	
Alternating Current	

## DIFFERENT TYPES OF WAVE

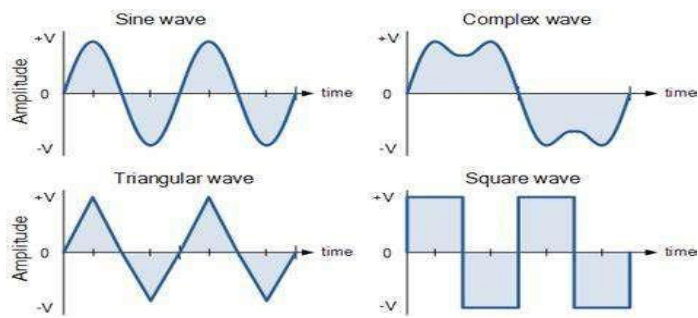


## BASIC ELECTRICAL SYMBOLS

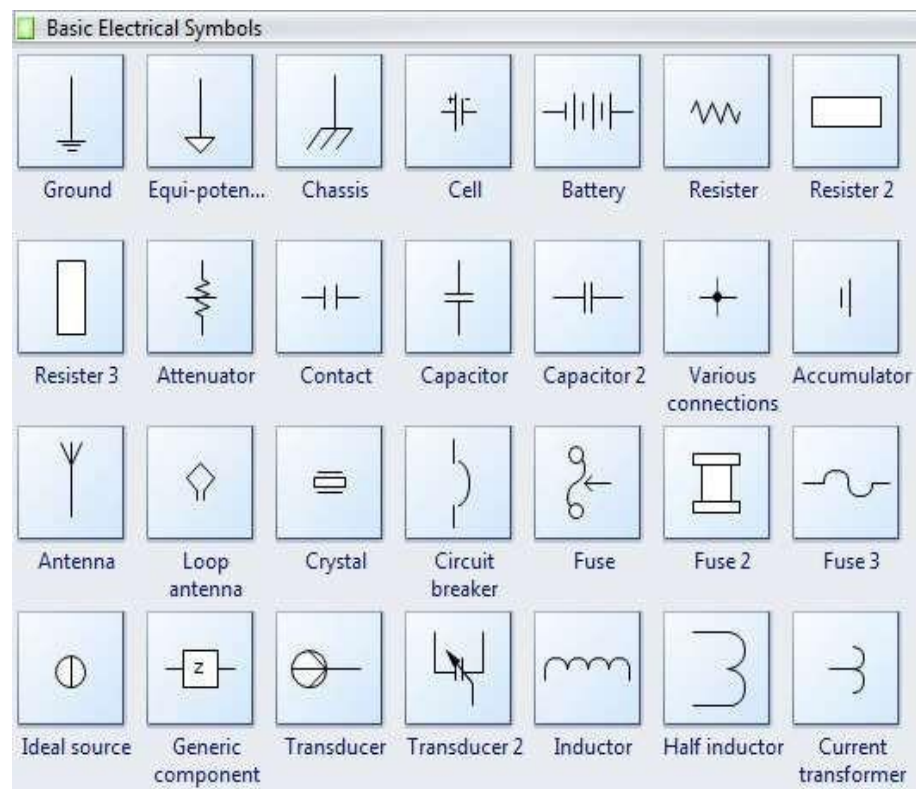


## RESISTANCE




# DIFFERENT TYPES OF CAPACITOR

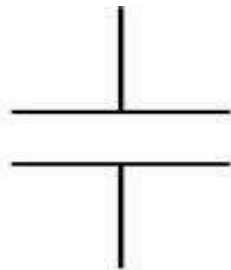

**Non-polarized  
Capacitor**

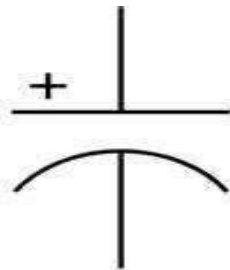

**Polarized  
Capacitor**

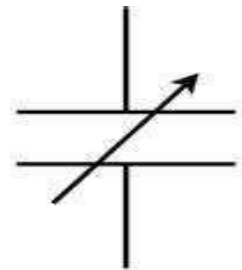

**Variable  
Capacitor**

# ENERGY SOURCES

## RENEWABLE ENERGY



Wind



Hydropower



Solar



Geothermal



Biomass

## NON-RENEWABLE ENERGY



Oil



Coal



Nuclear





Natural Gas

## ENERGY SOURCES

DESERTIFIACATION


LAND DEGRADATION

# Working of inductor

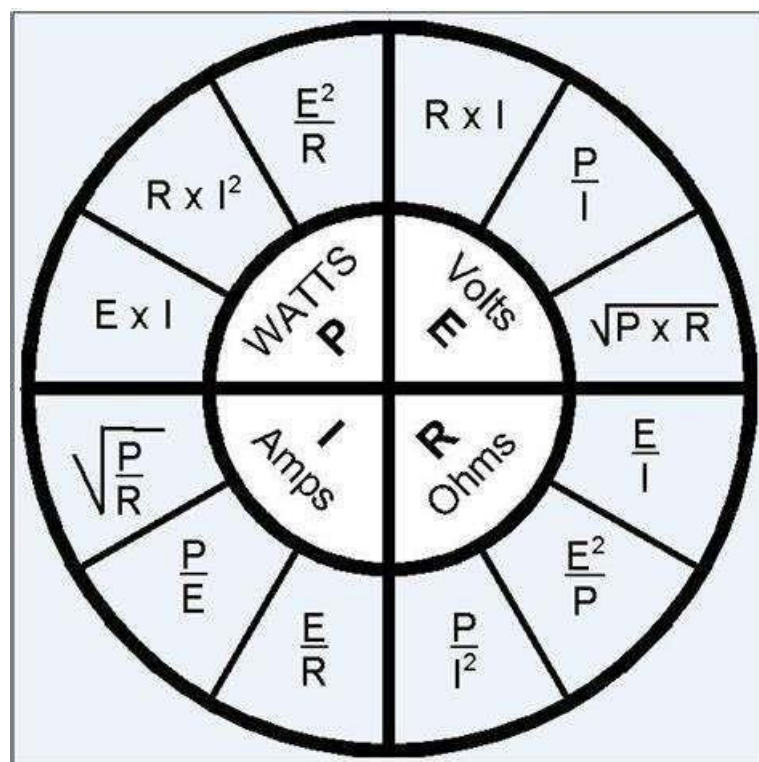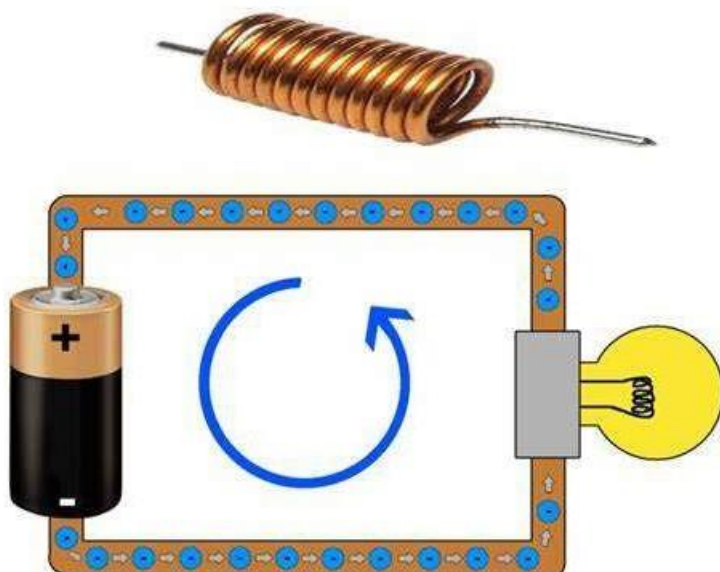



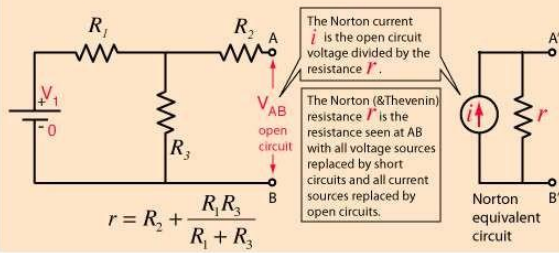
## Norton's Theorem

Any collection of batteries and resistances with two terminals is electrically equivalent to an ideal [current source](#)  $i$  in parallel with a single resistor  $r$ . The value of  $r$  is the same as that in the [Thevenin equivalent](#) and the current  $i$  can be found by dividing the open circuit voltage by  $r$ .



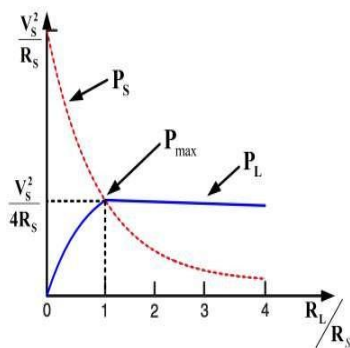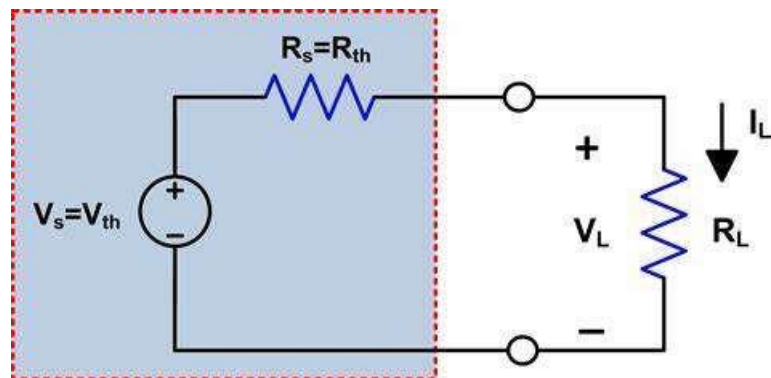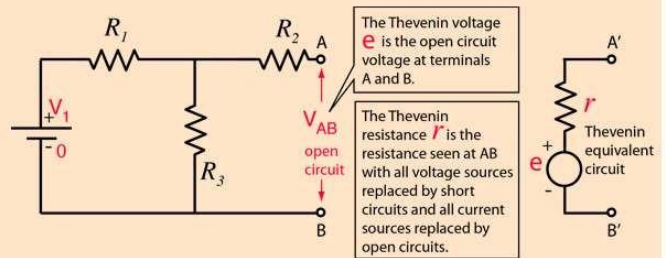
## Thevenin's Theorem


Any combination of batteries and resistances with two terminals can be replaced by a single [voltage source](#)  $e$  and a single series resistor  $r$ . The value of  $e$  is the open circuit voltage at the terminals, and the value of  $r$  is  $e$  divided by the current with the terminals short circuited.






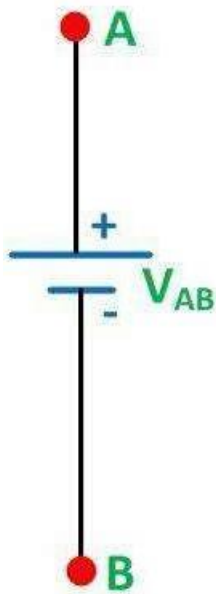


Circuit Globe

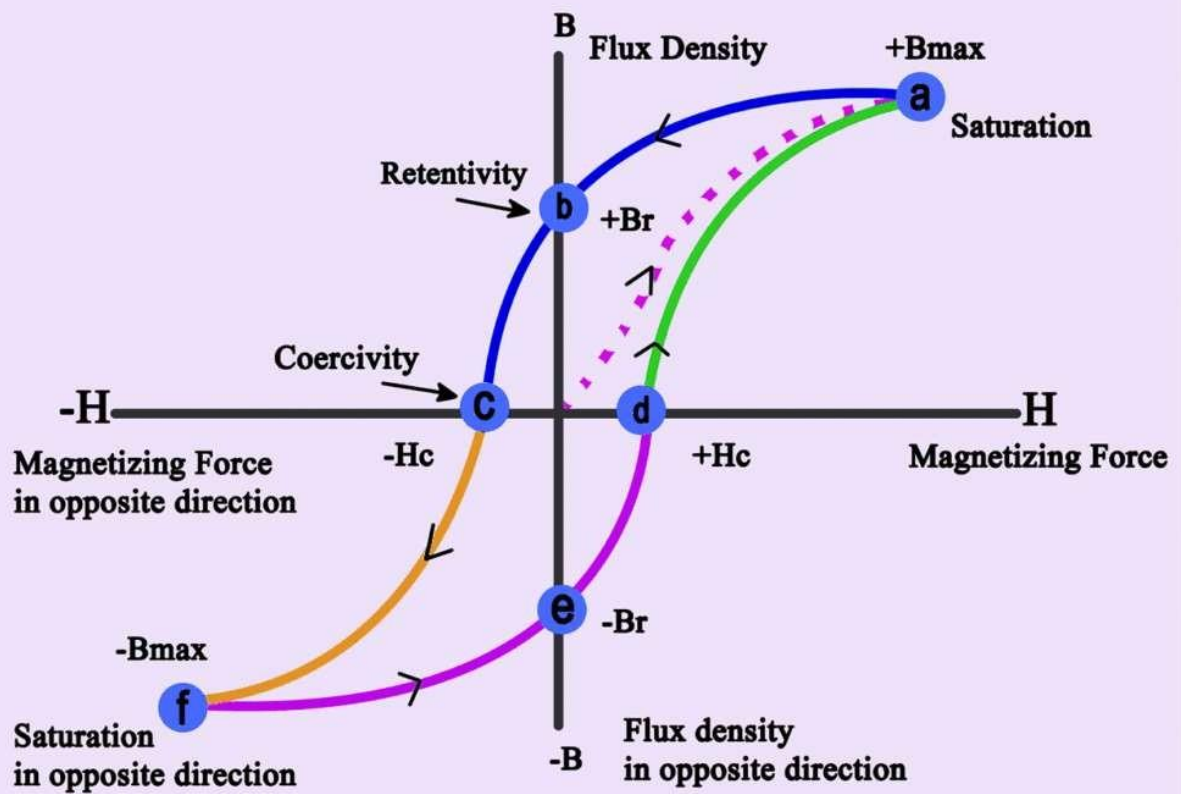




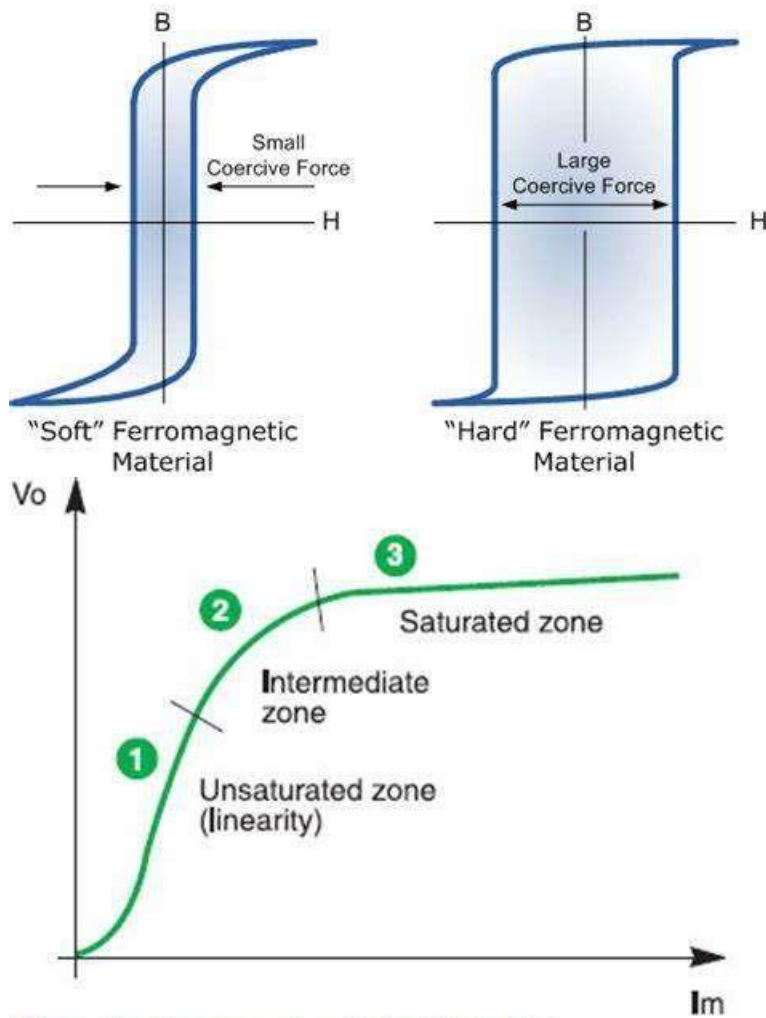

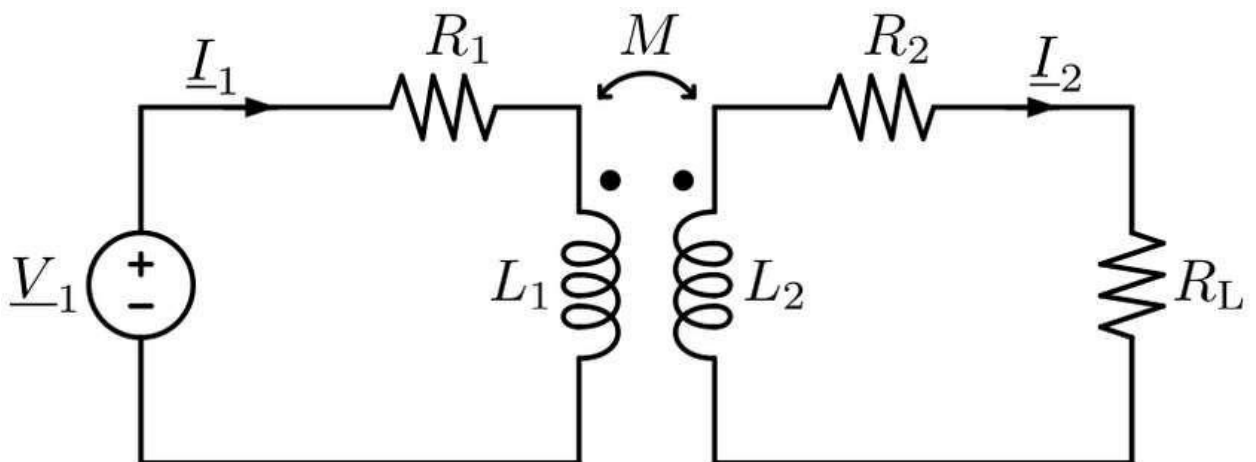Magnetization curve (excitation) for a CT.  
 Output voltage as a function of the magnetizing current.  
 $V_o = f(I_m)$



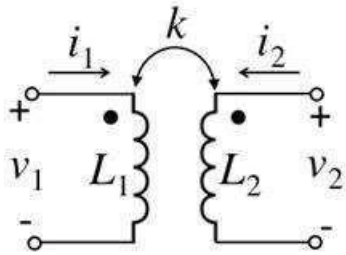

Time domain:

$$v_1 = L_1 \frac{di_1}{dt} + L_{12} \frac{di_2}{dt}$$

$$v_2 = L_{21} \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

Phasor domain:

$$V_1 = j\omega L_1 I_1 + j\omega L_{12} I_2$$

$$V_2 = j\omega L_{21} I_1 + j\omega L_2 I_2$$

where,  $L_{12} = L_{21} = \pm k \sqrt{L_1 L_2}$



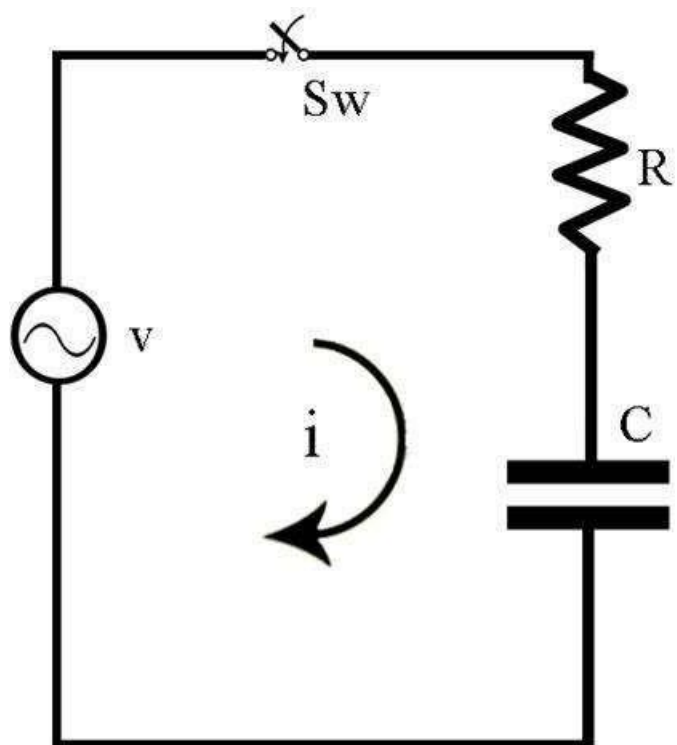
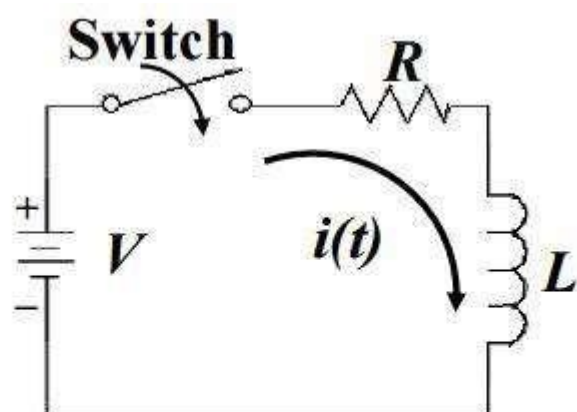


Figure: 1 Series R-C circuit

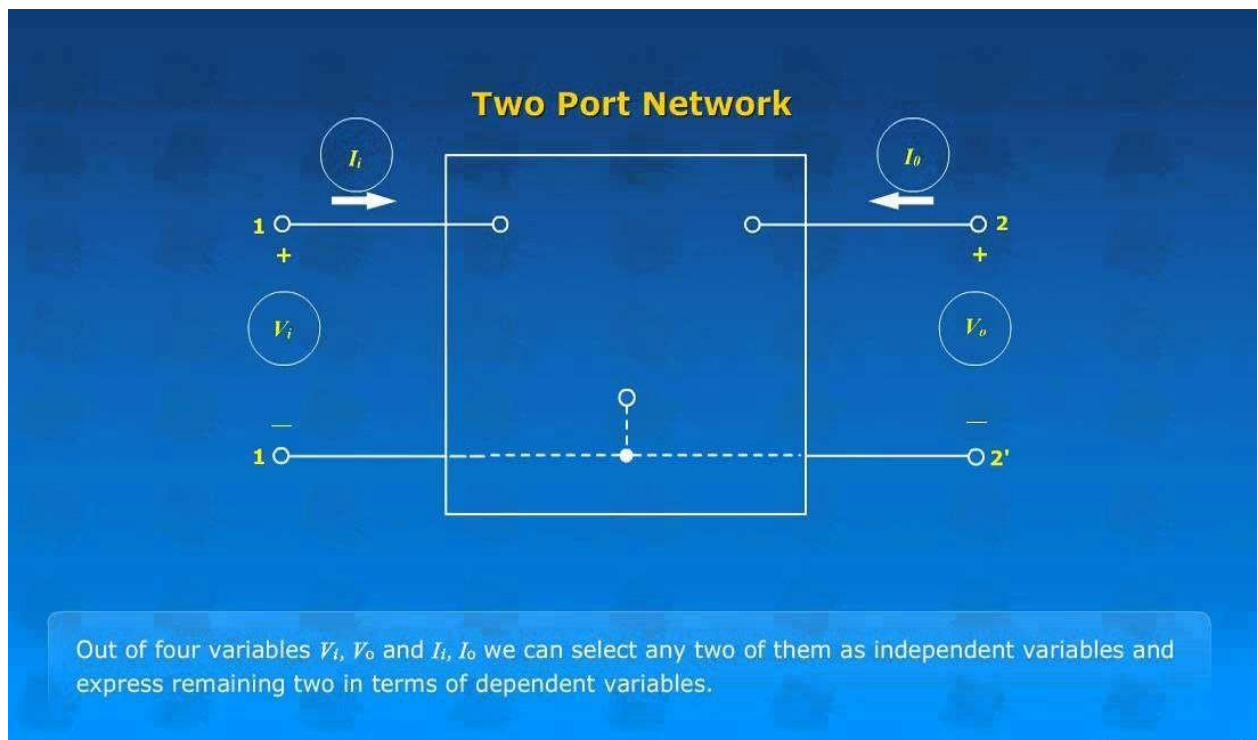


$$v_L(t) = Ve^{-(t/[L/R])} = Ve^{-(R/L)t}$$

## CHAPTER -6

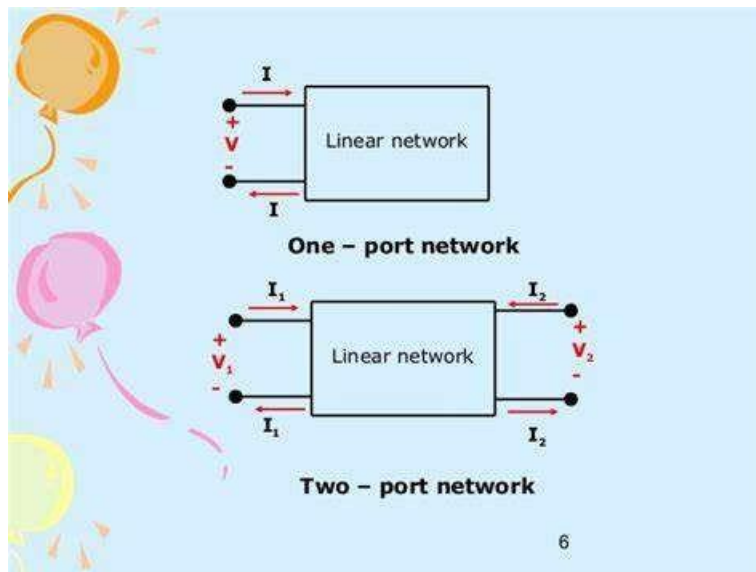

# Two-port Network Representation

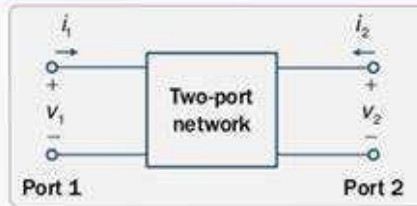

## ■ z-parameter

$$V_1 = Z_{11}i_1 + Z_{12}i_2$$

$$V_2 = Z_{21}i_1 + Z_{22}i_2$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

## ■ y-parameter

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

## ■ h-parameter

$$\begin{bmatrix} V_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ V_2 \end{bmatrix}$$

## ■ ABCD parameters

$$\begin{bmatrix} V_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -i_2 \end{bmatrix}$$