








GANDHI SCHOOL OF
ENGINEERING, BHABANDHA, BERHAMPUR

TEACHING AND LEARNING MATERIAL


SUBJECT: CIRCUIT THEORY
SEMESTER: 3RD

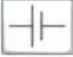CHAPTER-1


DIFFERENT TYPES OF POWER SOURCE

Power sources	
	Battery
	Battery with polarity labels
	Ideal current source
	Ideal voltage source
	Oscillator
	AC current source
	AC voltage source
	DC current source
	DC voltage source


DIFFERENT TYPES OF SOURCE

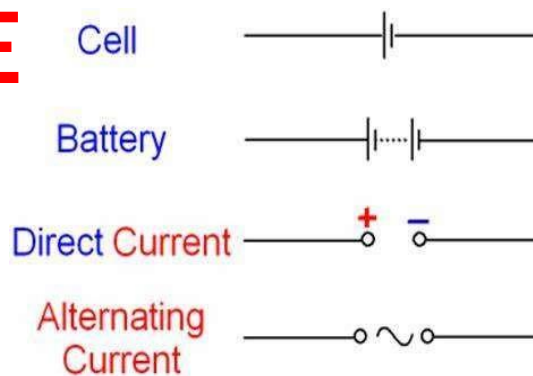

DIFFERENT TYPES OF WAVE

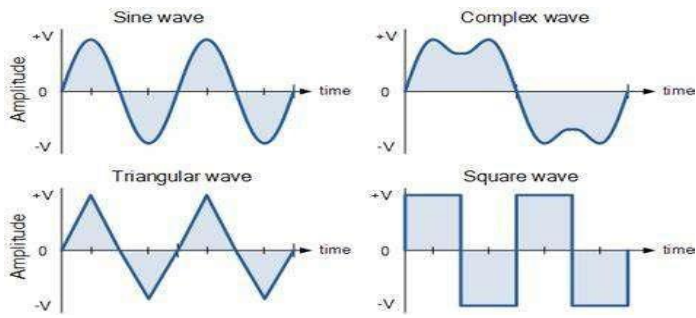


BASIC ELECTRICAL SYMBOLS

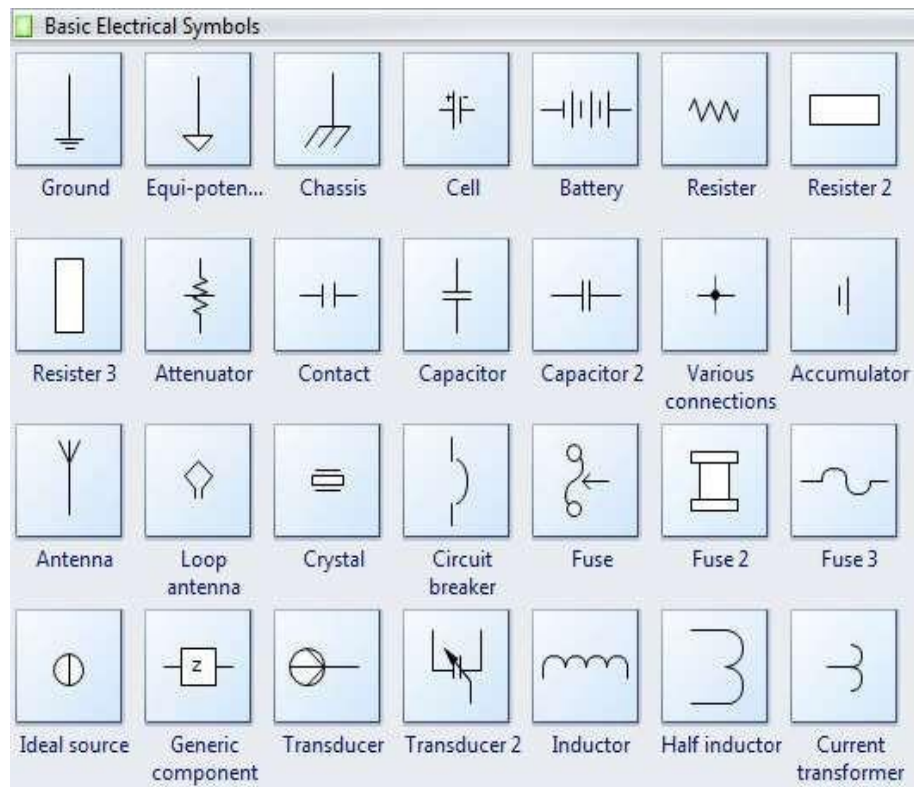


RESISTANCE




DIFFERENT TYPES OF CAPACITOR

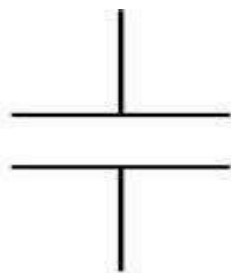

**Non-polarized
Capacitor**

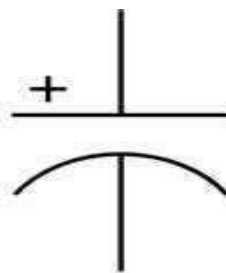

**Polarized
Capacitor**

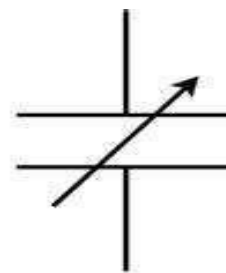

**Variable
Capacitor**

ENERGY SOURCES


RENEWABLE ENERGY



Wind



Hydropower

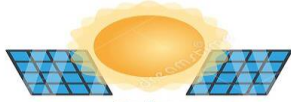

Solar



Geothermal



Biomass

NON-RENEWABLE ENERGY



Oil



Coal



Nuclear





Natural Gas

ENERGY SOURCES

DESERTIFICATION


LAND DEGRADATION

Working of inductor

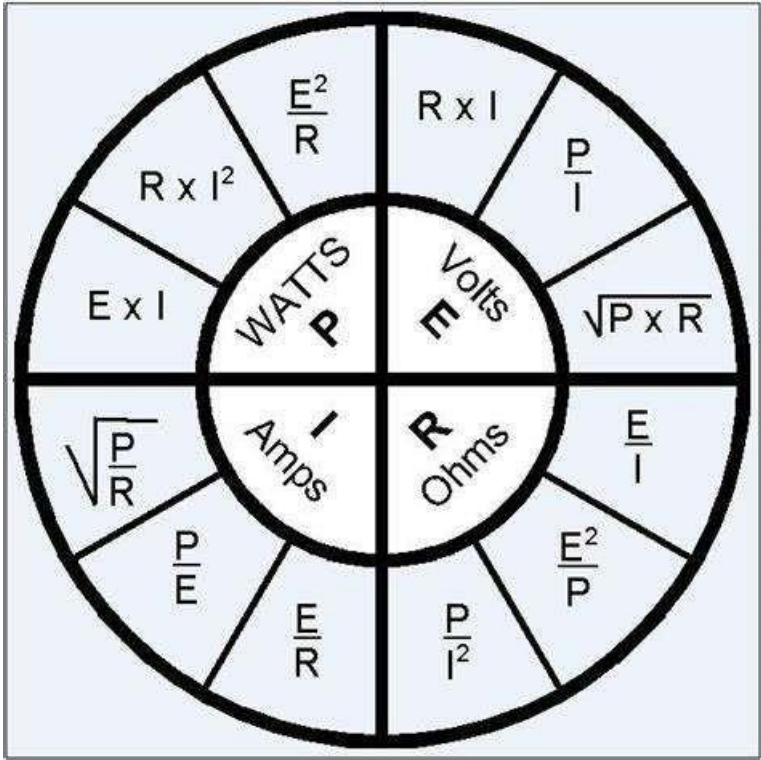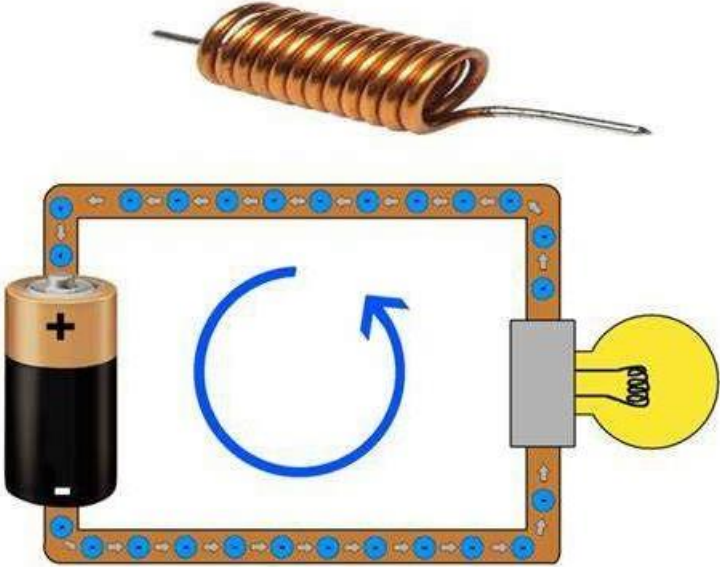




Norton's Theorem

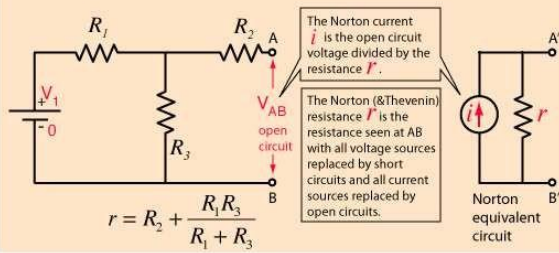
Any collection of batteries and resistances with two terminals is electrically equivalent to an ideal [current source](#) i in parallel with a single resistor r . The value of r is the same as that in the [Thevenin equivalent](#) and the current i can be found by dividing the open circuit voltage by r .




Thevenin's Theorem

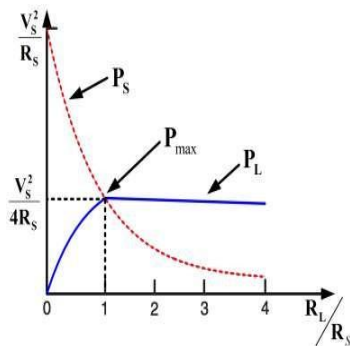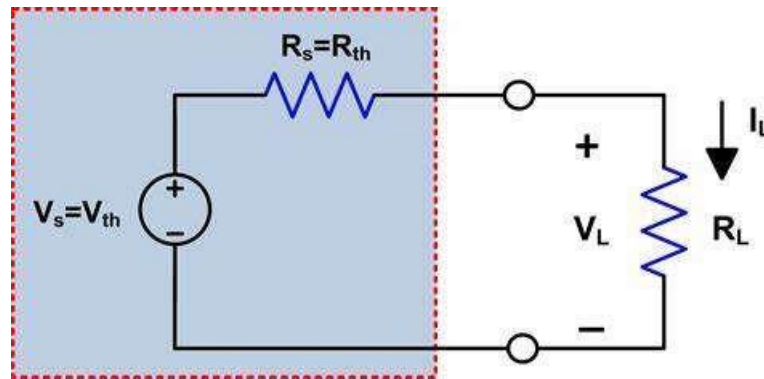
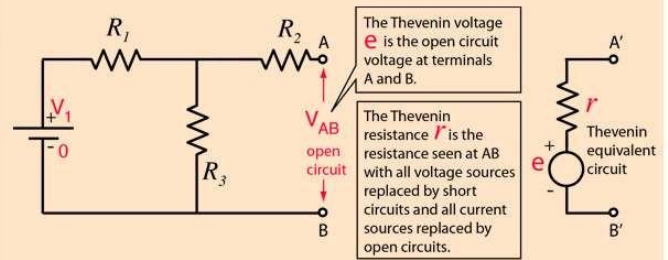
Any combination of batteries and resistances with two terminals can be replaced by a single [voltage source](#) e and a single series resistor r . The value of e is the open circuit voltage at the terminals, and the value of r is e divided by the current with the terminals short circuited.



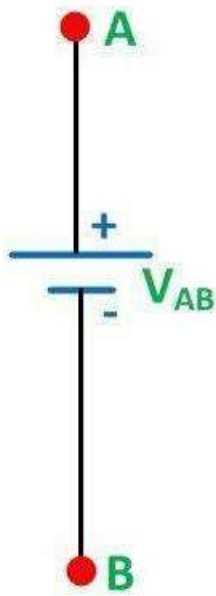



Circuit Globe

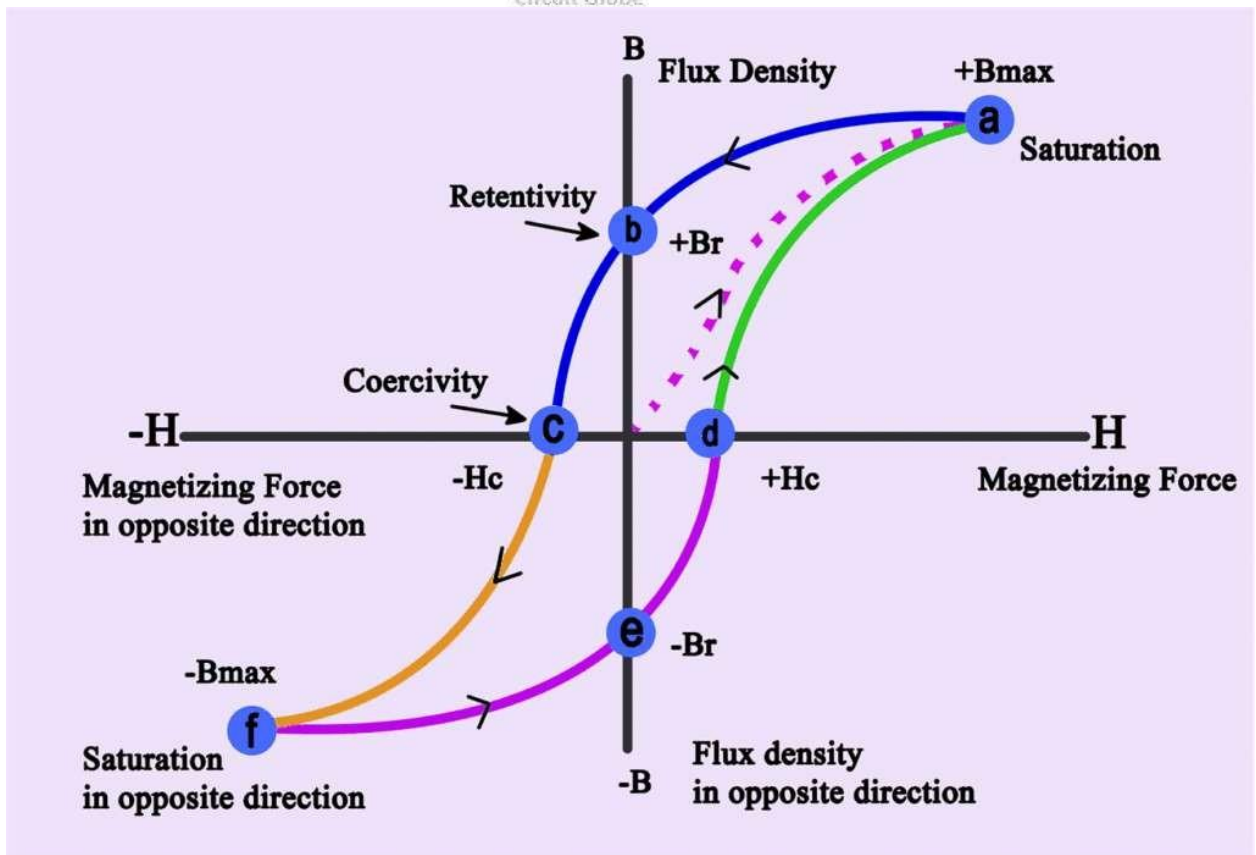

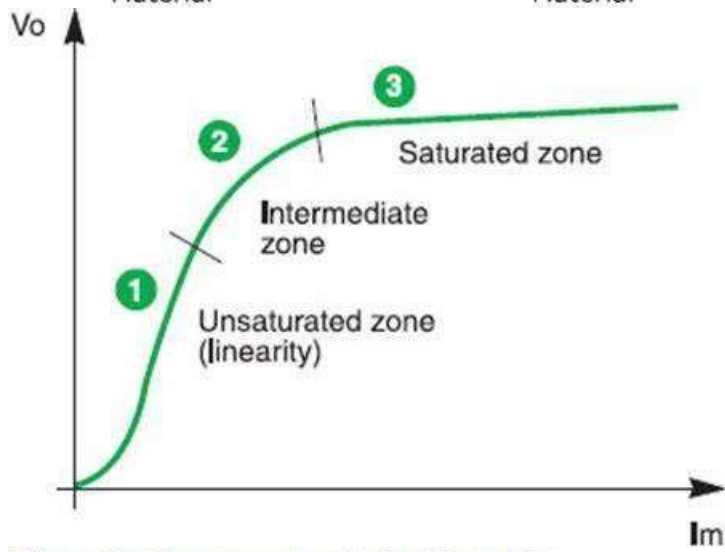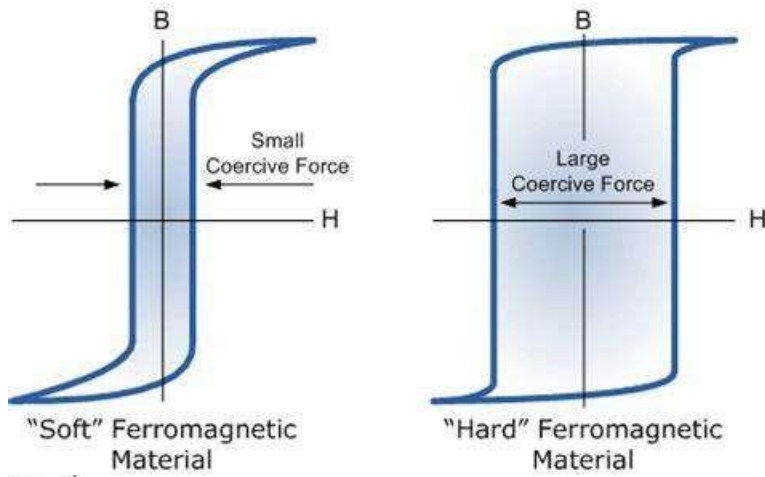

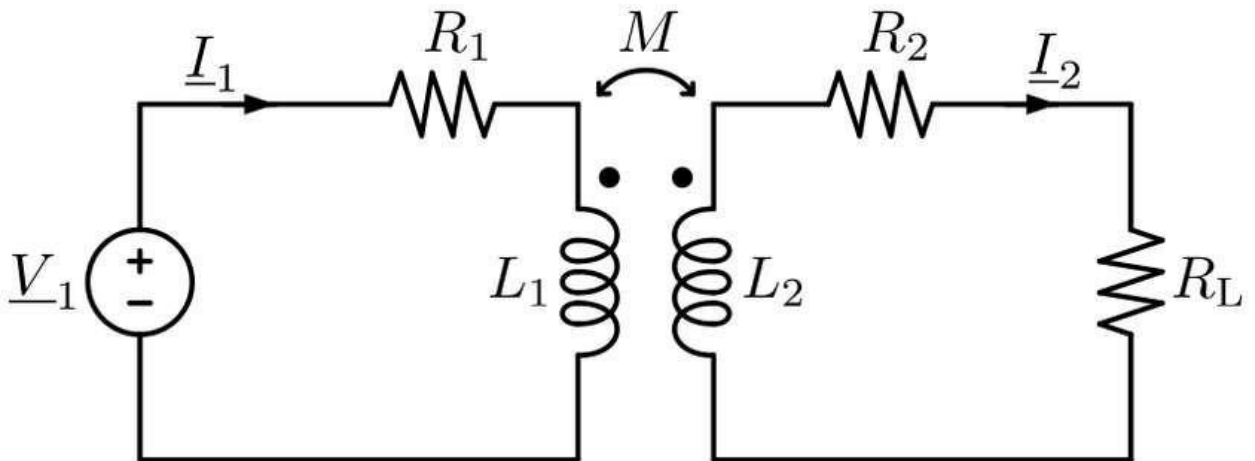Magnetization curve (excitation) for a CT.
 Output voltage as a function of the magnetizing current.
 $V_o = f(I_m)$



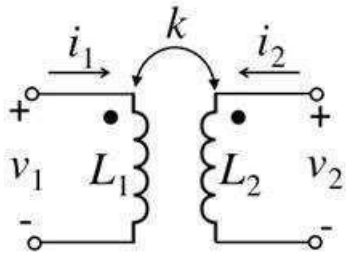

Time domain:

$$v_1 = L_1 \frac{di_1}{dt} + L_{12} \frac{di_2}{dt}$$

$$v_2 = L_{21} \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

Phasor domain:

$$V_1 = j\omega L_1 I_1 + j\omega L_{12} I_2$$

$$V_2 = j\omega L_{21} I_1 + j\omega L_2 I_2$$

where, $L_{12} = L_{21} = \pm k \sqrt{L_1 L_2}$



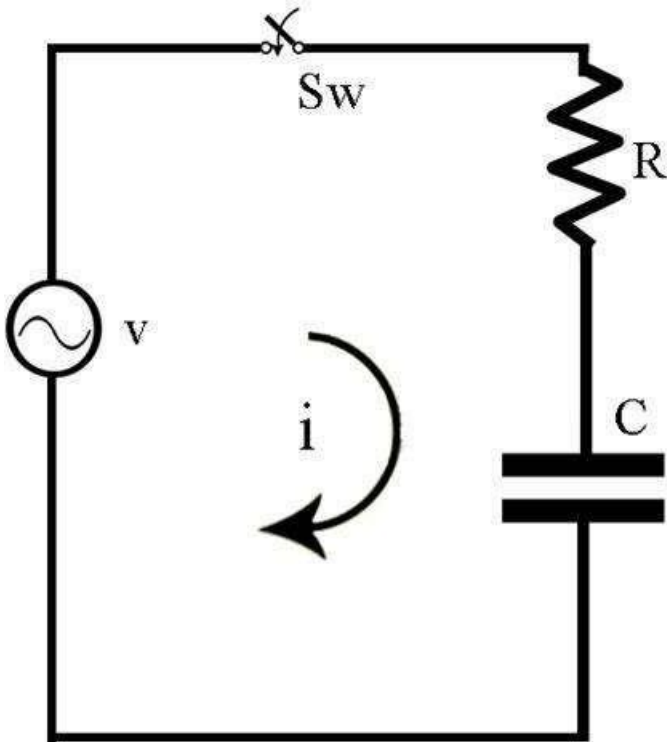
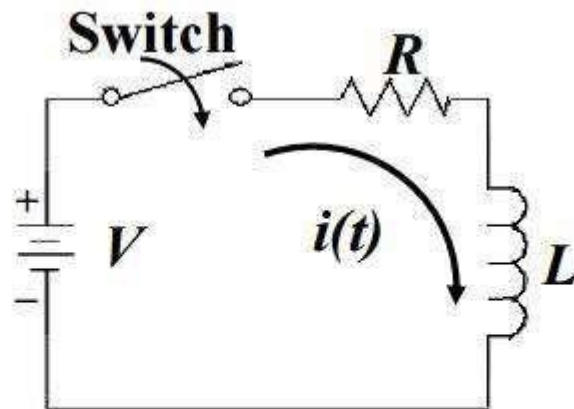


Figure: 1 Series R-C circuit

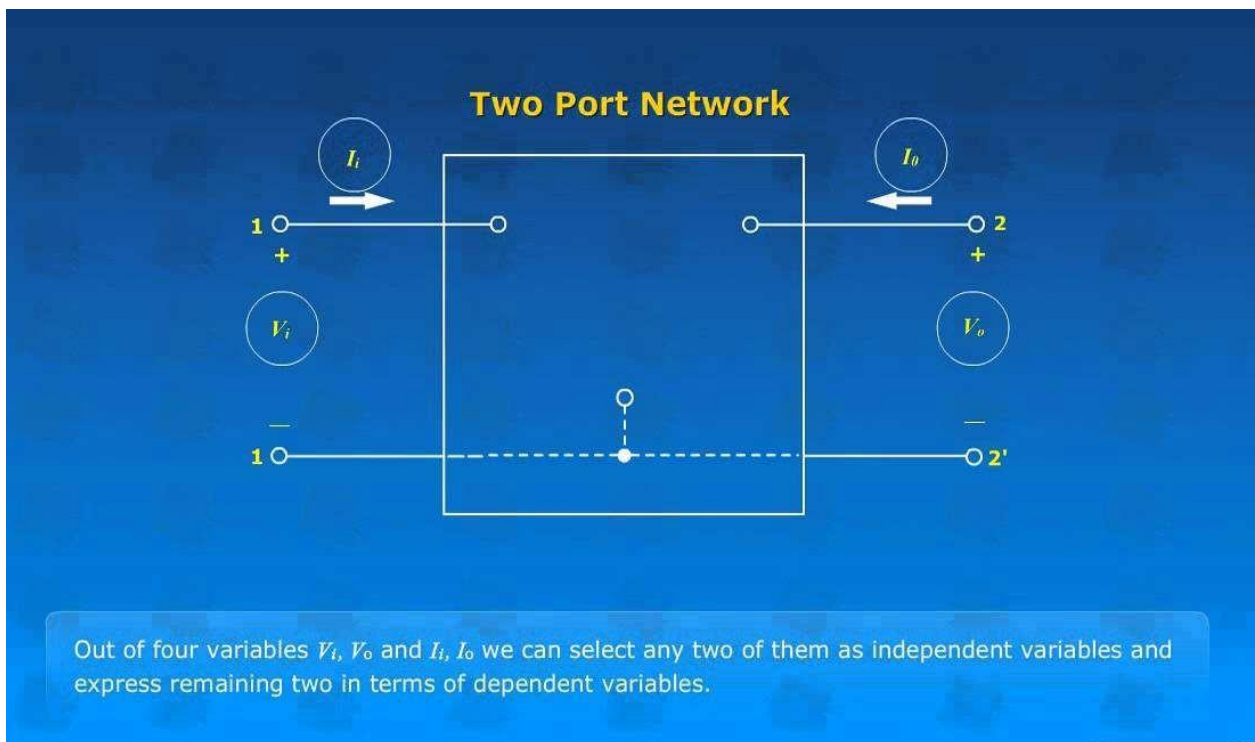


$$v_L(t) = Ve^{-(t/[L/R])} = Ve^{-(R/L)t}$$

CHAPTER -6

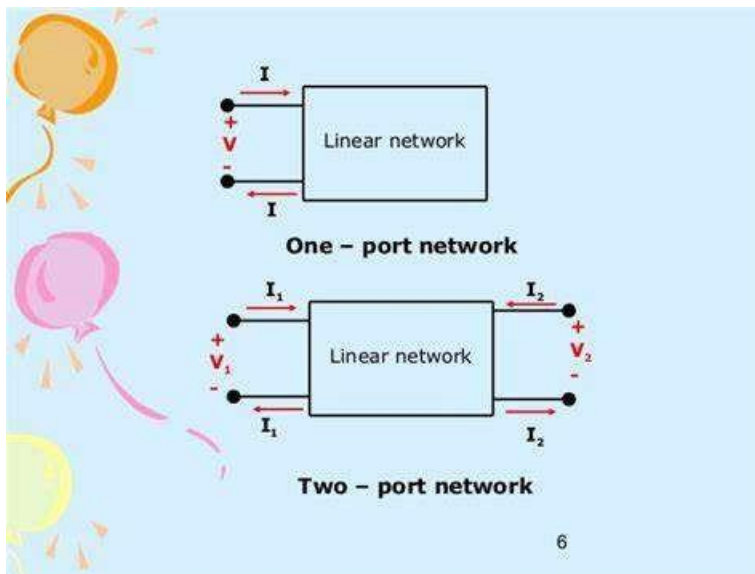

Two-port Network Representation

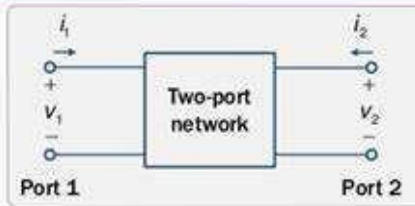

■ z-parameter

$$v_1 = z_{11}i_1 + z_{12}i_2$$

$$v_2 = z_{21}i_1 + z_{22}i_2$$

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

■ y-parameter

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

■ h-parameter

$$\begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ v_2 \end{bmatrix}$$

■ ABCD parameters

$$\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} v_2 \\ -i_2 \end{bmatrix}$$