



GANDHI SCHOOL OF
ENGINEERING, BHABANDHA, BERHAMPUR





TEACHING AND LEARNING MATERIAL

SUBJECT: ANALOG ELECTRONICS &
OP-AMP
SEMESTER: 4TH

PREPARED BY: SATYABRATA TRIPATHY

Unit-1: DIODE, TRANSISTORS AND CIRCUITS

DIODE

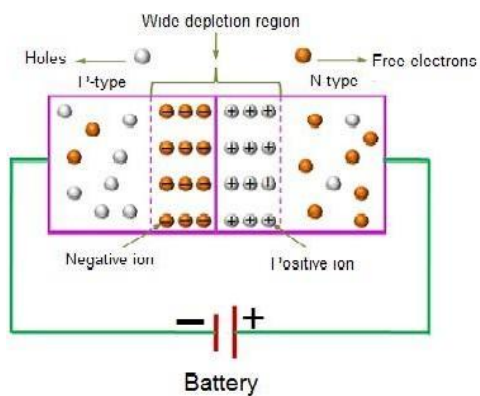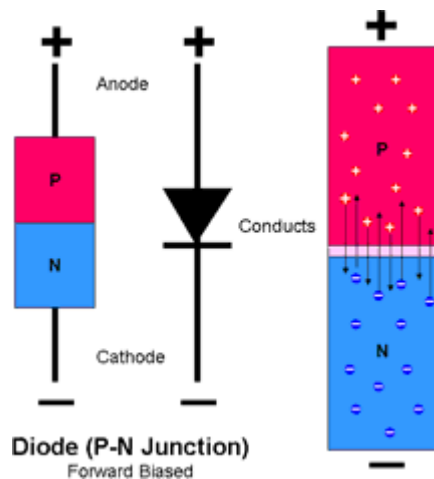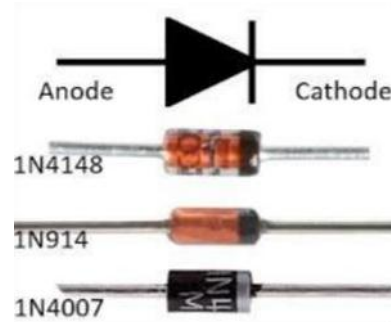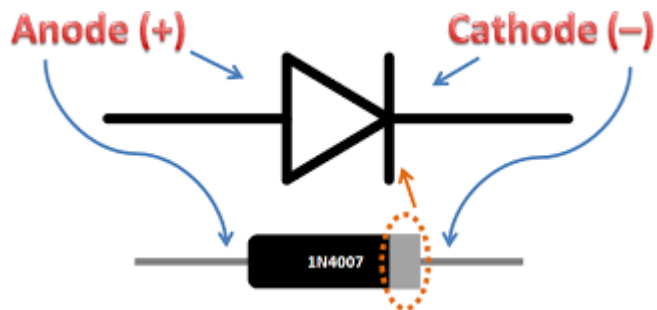

ZENER DIODE

What is a ZENER DIODE?


A **Zener diode** is designed to have a specific breakdown voltage, so that it will conduct current in reverse when the cathode reaches its threshold voltage. The breakdown voltage can be as low as 2.4V to as high as 1kV.

Applications

Some common uses for Zener diodes in circuits:

- Voltage regulation
- As a voltage reference
- Surge suppressors
- Switching signals
- Clipping waveforms


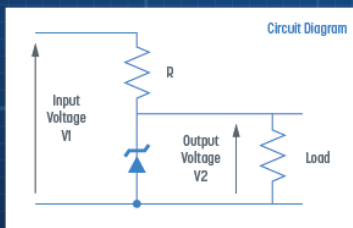
Cathode: The cathode is typically connected to a positive voltage. The zener diode will not conduct electricity from cathode to anode until the breakdown voltage is reached.



Anode: The anode is typically connected to ground. If a positive voltage is applied to the anode, it will conduct like a regular diode.


Zener Diode



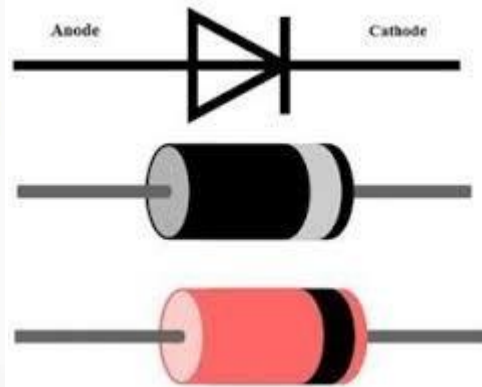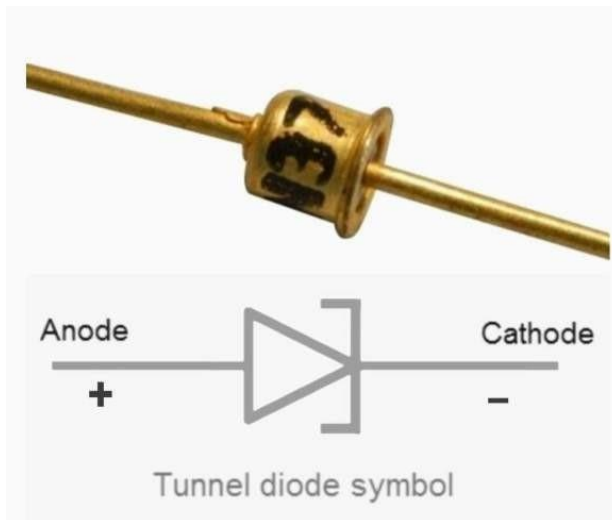

UNIT-2


HALF WAVE RECTIFIER

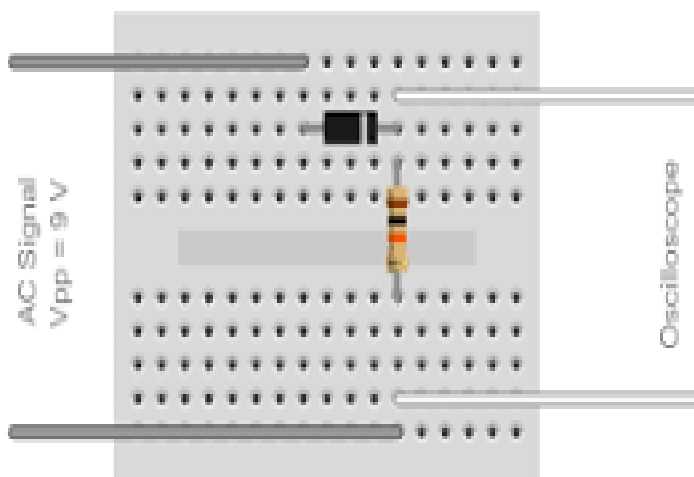


Made with
Fritzing



CENTRE TAP FULL WAVE RECTIFIER

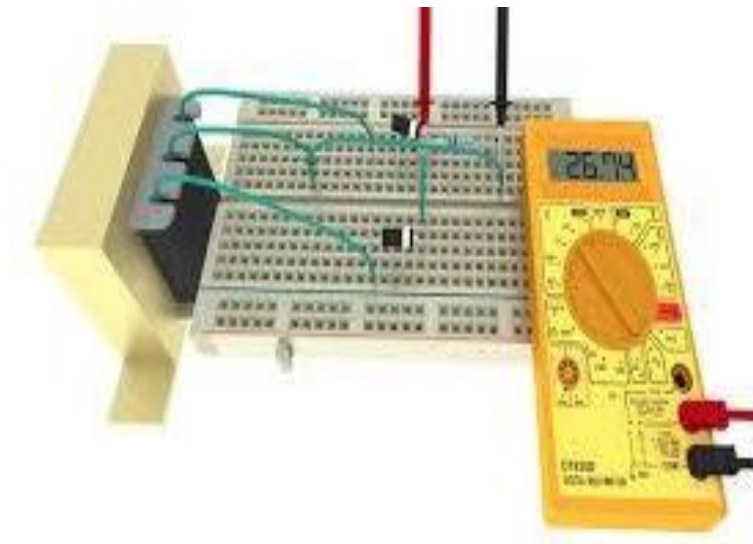


FULL WAVE BRIDGE RECTIFIER

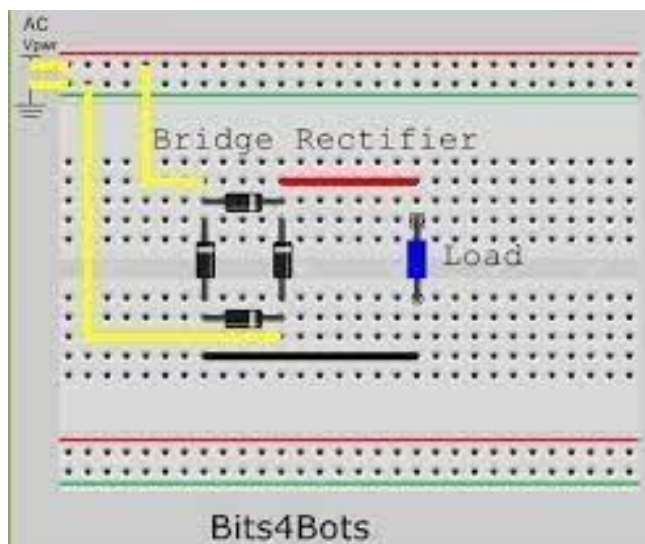


UNIT-3

BJT

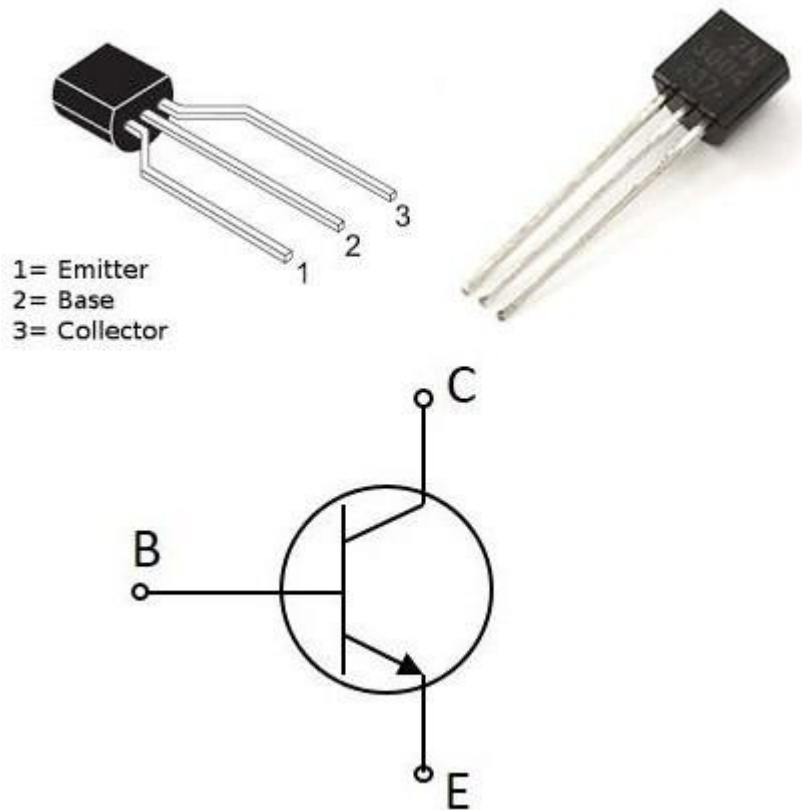


UNIT-4

FET

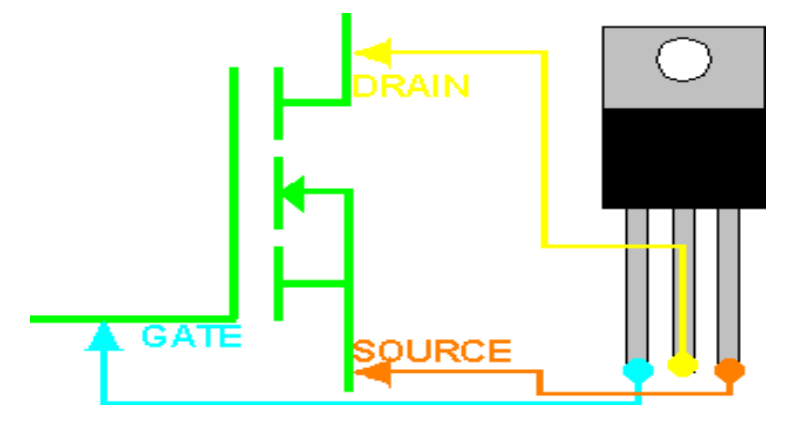

BJT V/S FET

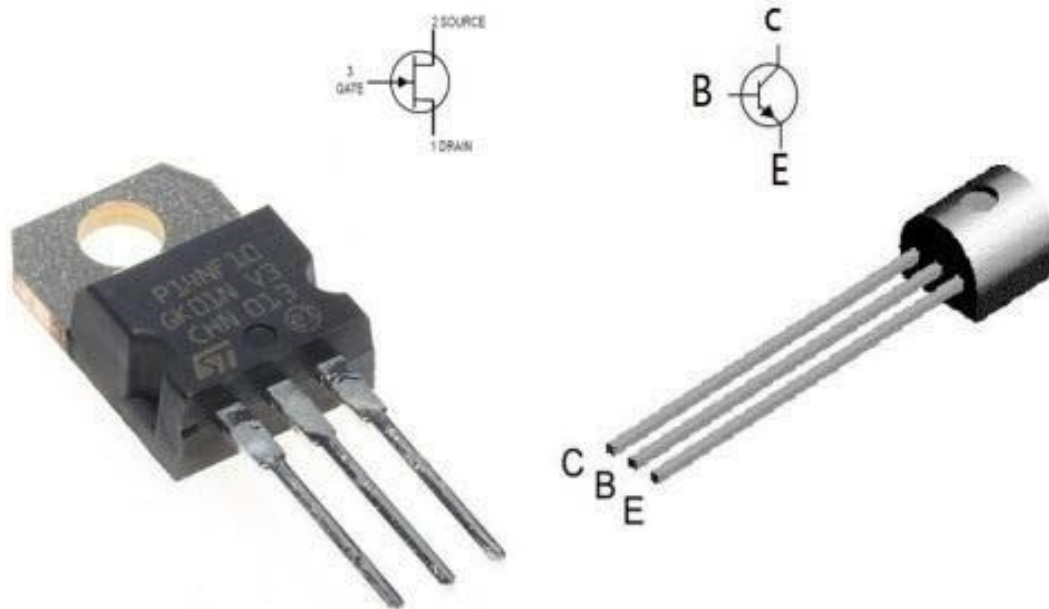

UNIT-8

OPAMP


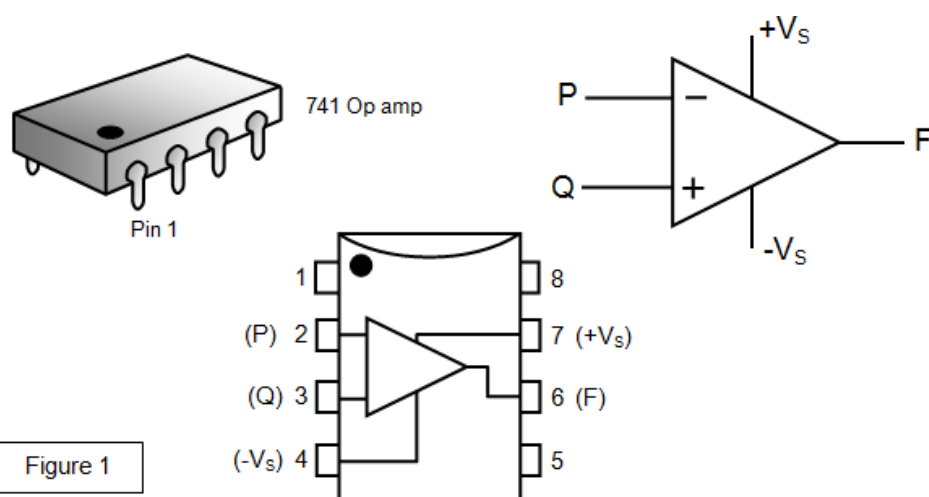


Figure 1

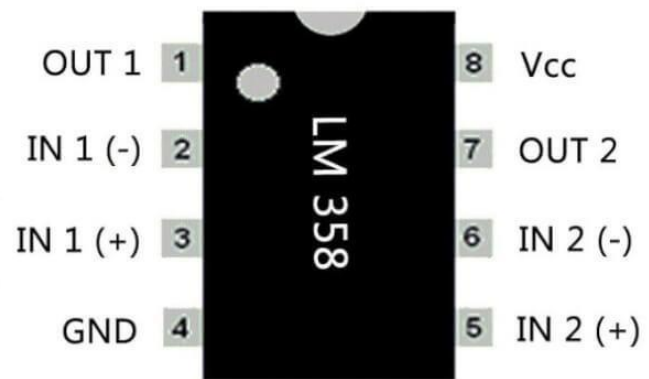

envirementalb.com